

---

# E40M

## Bode Plots, dB


# Reading

---

- Reader
  - 7.1-7.2 – Bode Plots

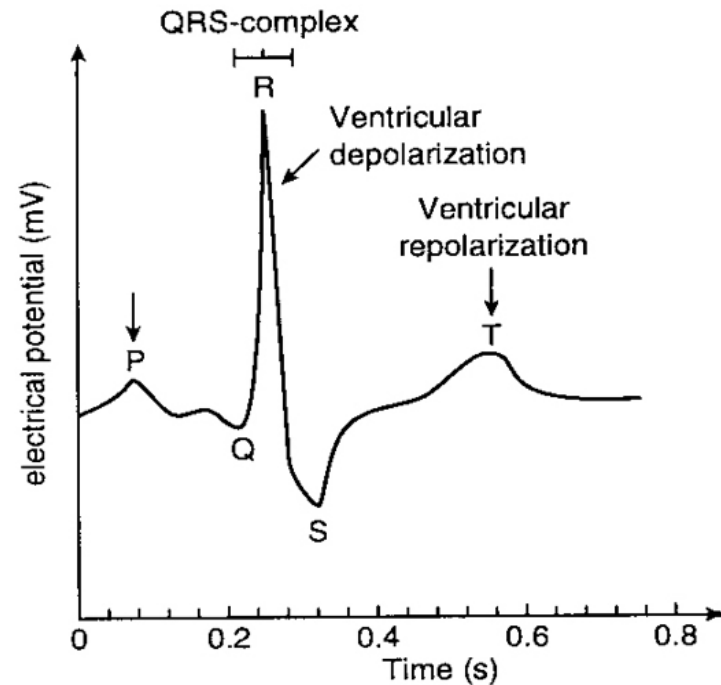
# EKG Lab

- Concepts
  - Amplifiers
  - Impedance
  - Noise
  - Safety
  - Filters
- Components
  - Capacitors
  - Inductors
  - Instrumentation and Operational Amplifiers




In this project we will build an electrocardiogram (ECG or EKG). This is a noninvasive device that measures the electrical activity of the heart using electrodes placed on the skin.
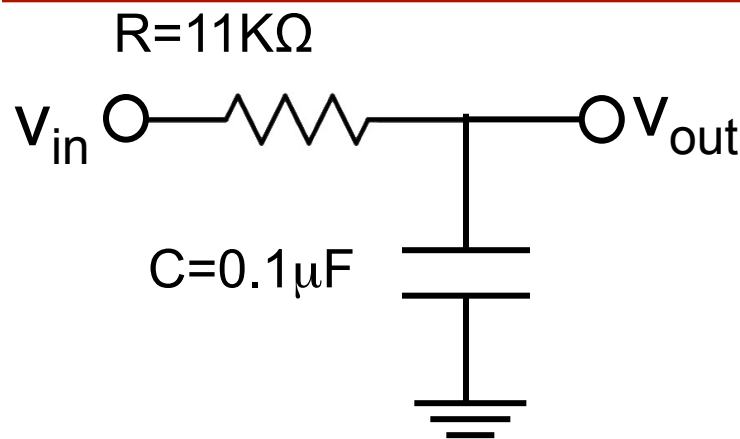
# Analyzing RC Circuits Using Impedance – Review (Low Pass Filter)




$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j*2\pi FC}} = \frac{1}{1 + j*2\pi FRC}$$

Gain vs. Freq

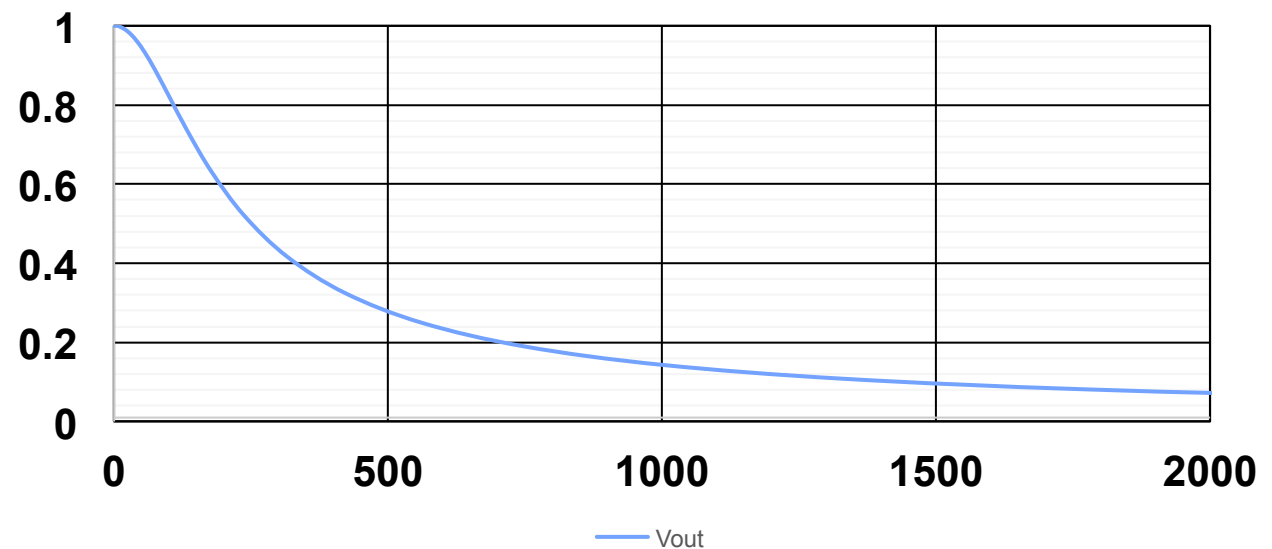

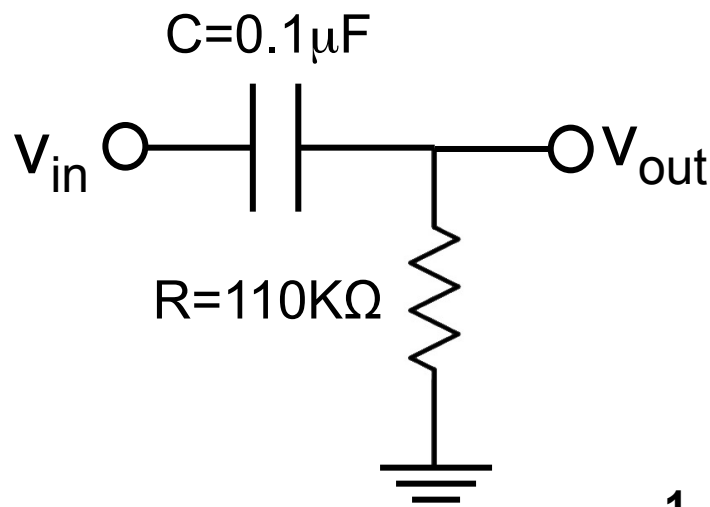
# Analyzing RC Circuits Using Impedance – Review (High Pass Filter)




$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j * 2\pi F C}} = \frac{j * 2\pi F R C}{1 + j * 2\pi F R C}$$

$RC = 11\text{ms}$ ;  $2\pi RC$  is about  $70\text{ms}$

Gain vs. Freq

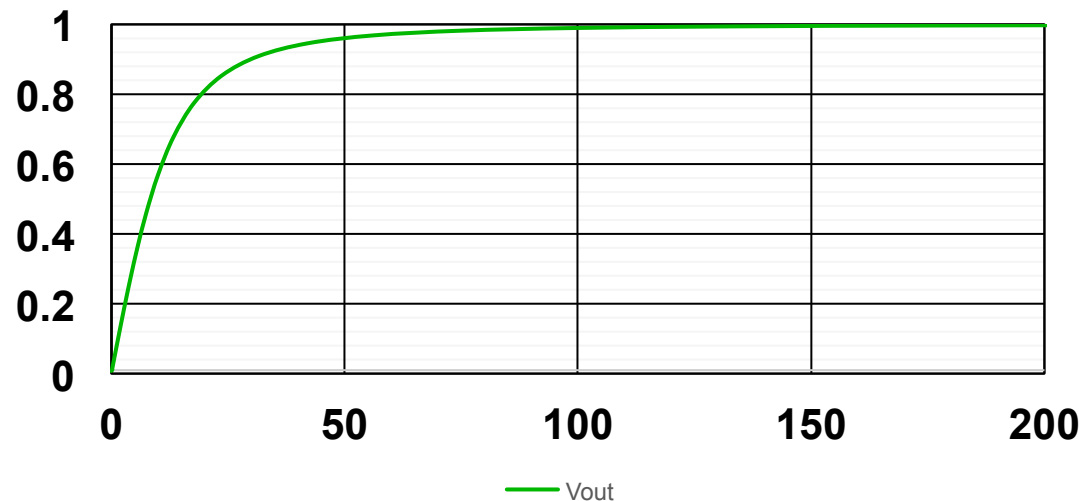

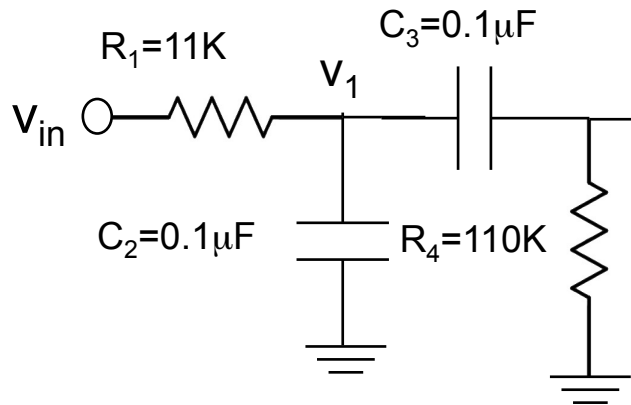
# Analyzing RC Circuits Using Impedance – Review (Band Pass Filter)



$$\frac{V_{out}}{V_{in}} = \frac{j * 2\pi F R_4 C_3}{1 + j * 2\pi F (R_4 C_3 + R_1 C_2 + R_1 C_3) + (j * 2\pi F)^2 R_1 C_2 R_4 C_3}$$

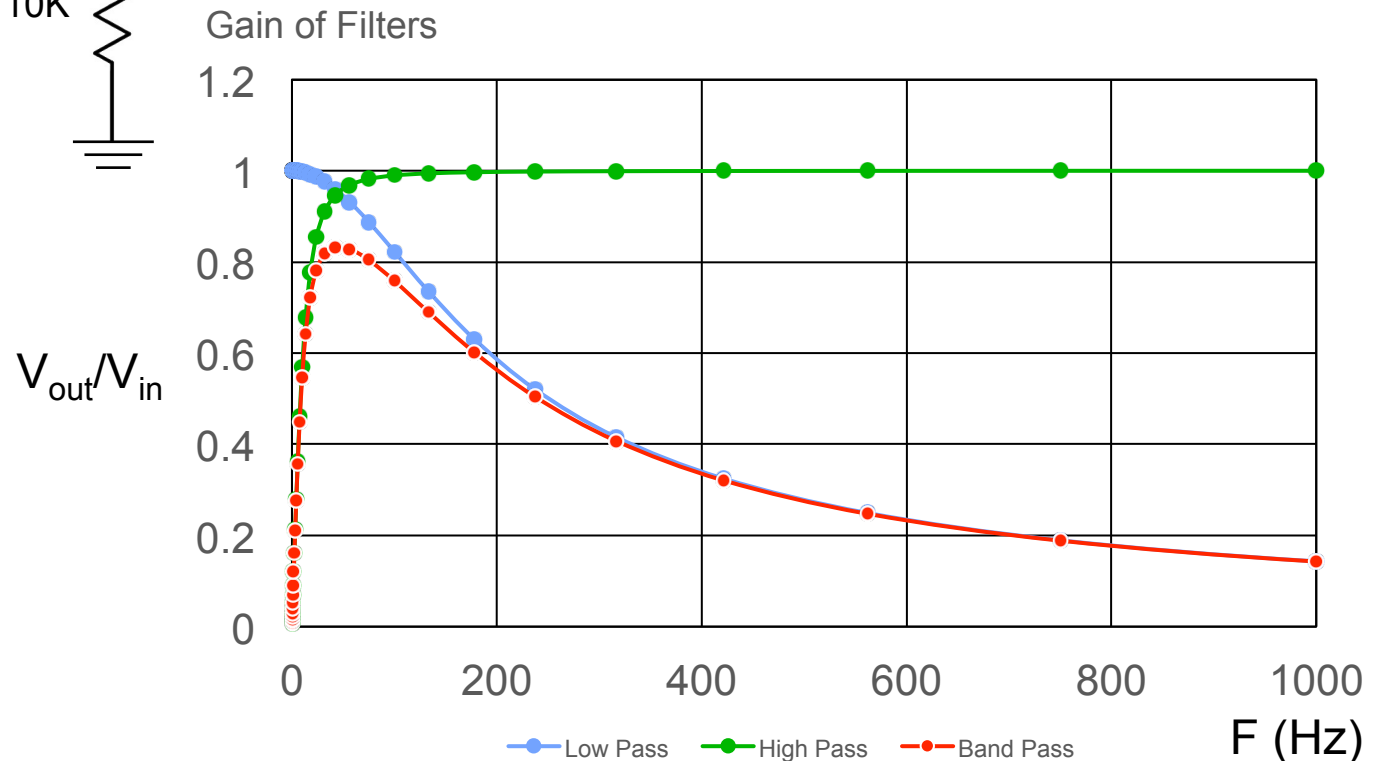- We'll use a filter that operates like this in the ECG lab project.




---

# BODE PLOTS

# Our Plots Are Not Very Good

- Most of the plot is for the “high frequency”
  - Your ear is very interested in each octave (2x) in freq
  - If you plot the full audio spectrum (20-20kHz)
    - 50% of the plot will be from 10-20kHz
      - And that is only one octave of ten!
    - You won’t be able to see the first five octaves!


Gain of Filters

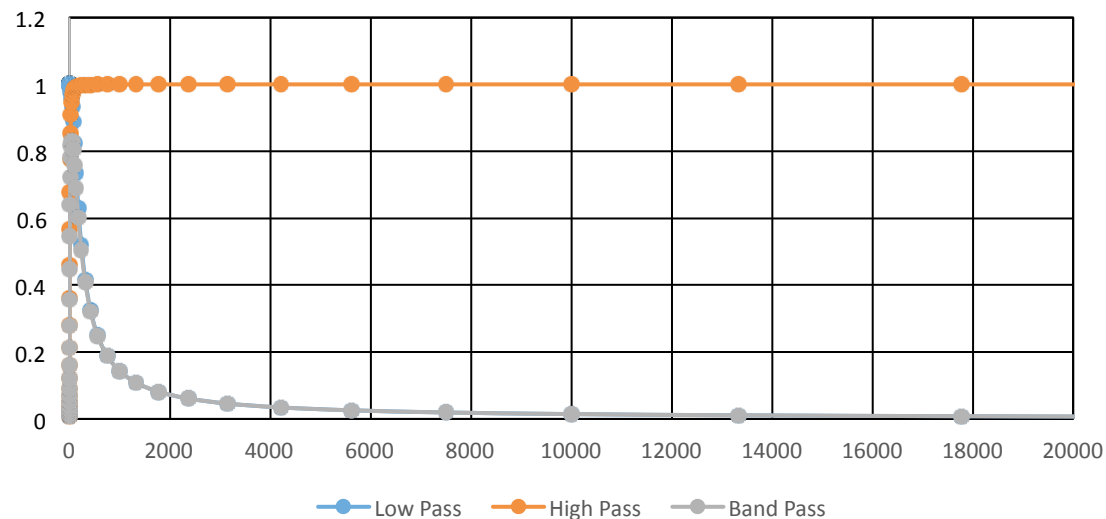



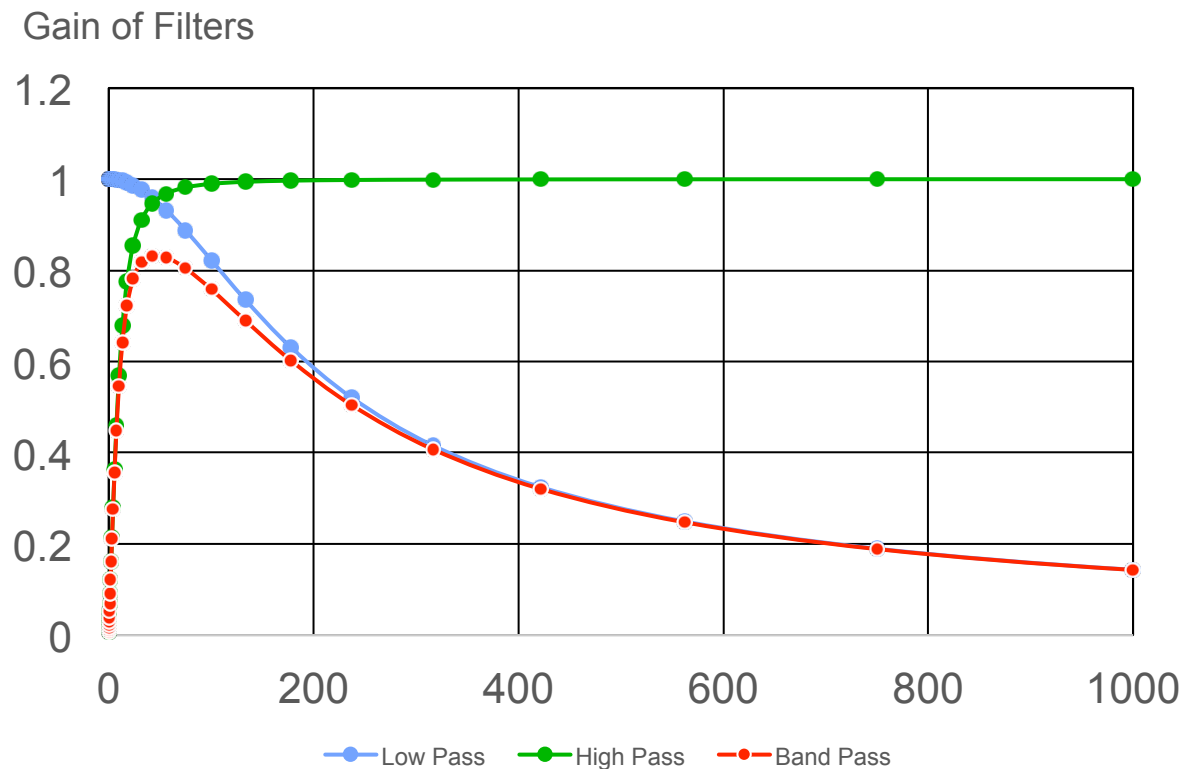
## More Plot Issues

- The plots usually are proportional to:
  - Constant, or  $F$  or  $F^{-1}$  or  $F^2$  or  $F^{-2}$
  - It would be great if these were easy to see on a plot



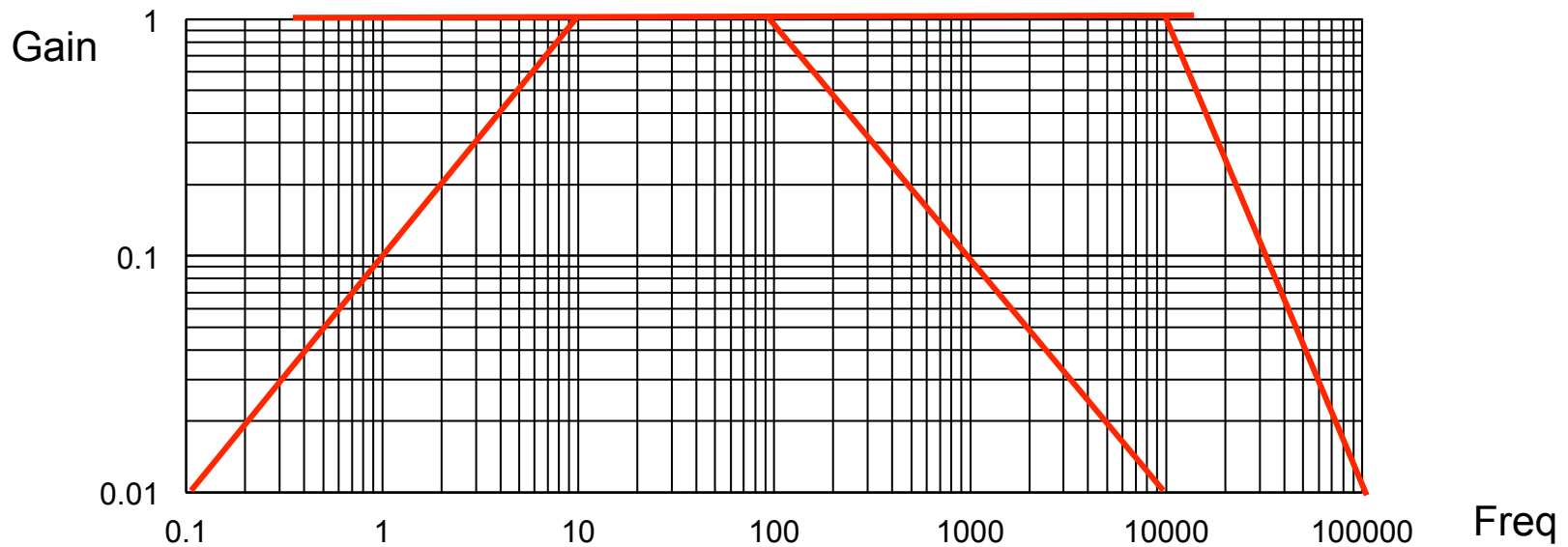
# There is an Easy Way to Fix Both Issues

- Use a log-log plot
  - That is plot the  $\log(\text{Gain})$  vs  $\log(F)$
  - Usually labeled with Gain and F
    - But the spacing between numbers is their log
- Any power of F is a straight line  $\log(F^n) = n * \log(F)$   
So the slope of the line is the power of F





## Example – Low Pass Filter

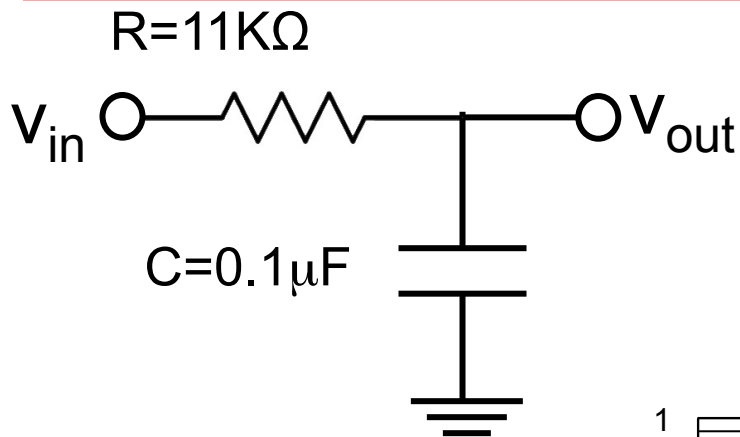


$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j * 2\pi FC}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF / F_c}$$

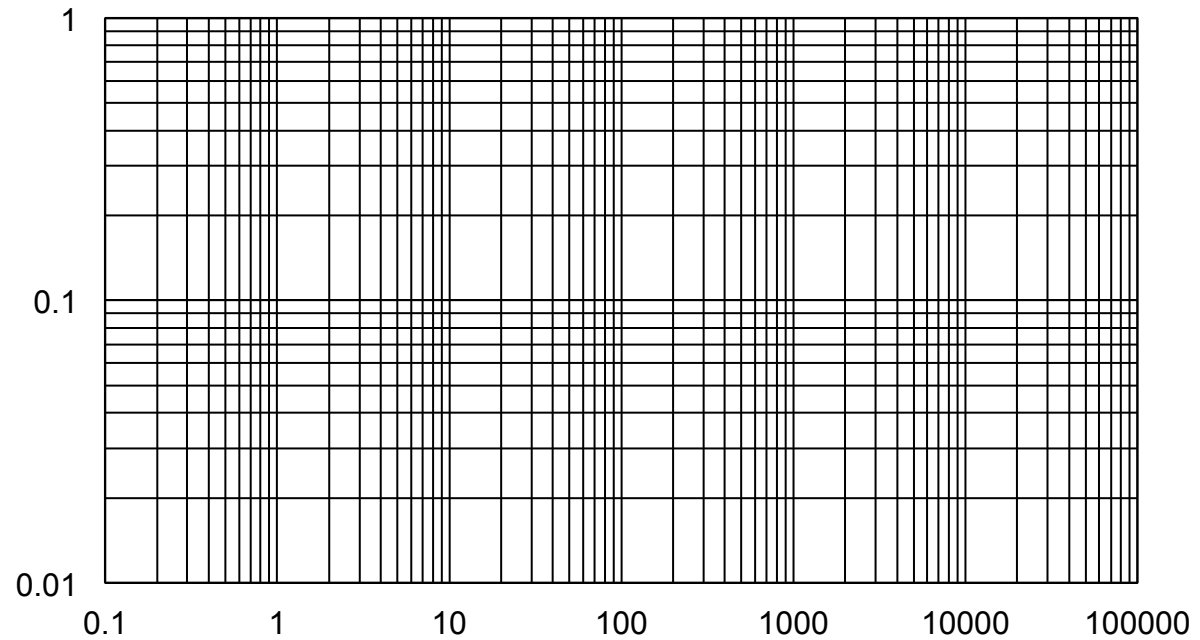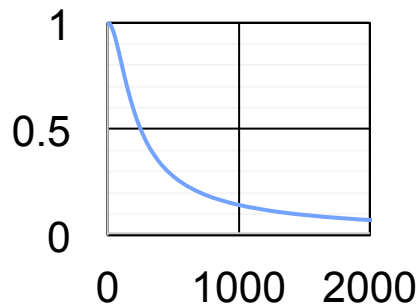$2\pi RC$  is about 7ms;  $F_c = 140\text{Hz}$





# Low Pass

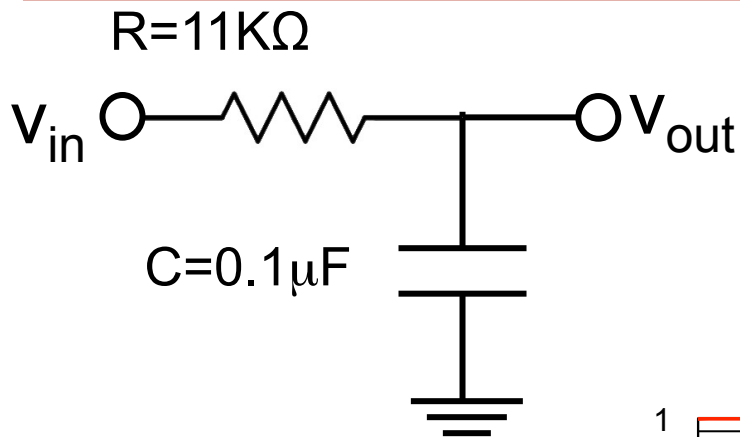


$$\frac{V_{out}}{V_{in}} = \frac{1}{R + \frac{1}{j * 2\pi FC}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF / F_c}$$

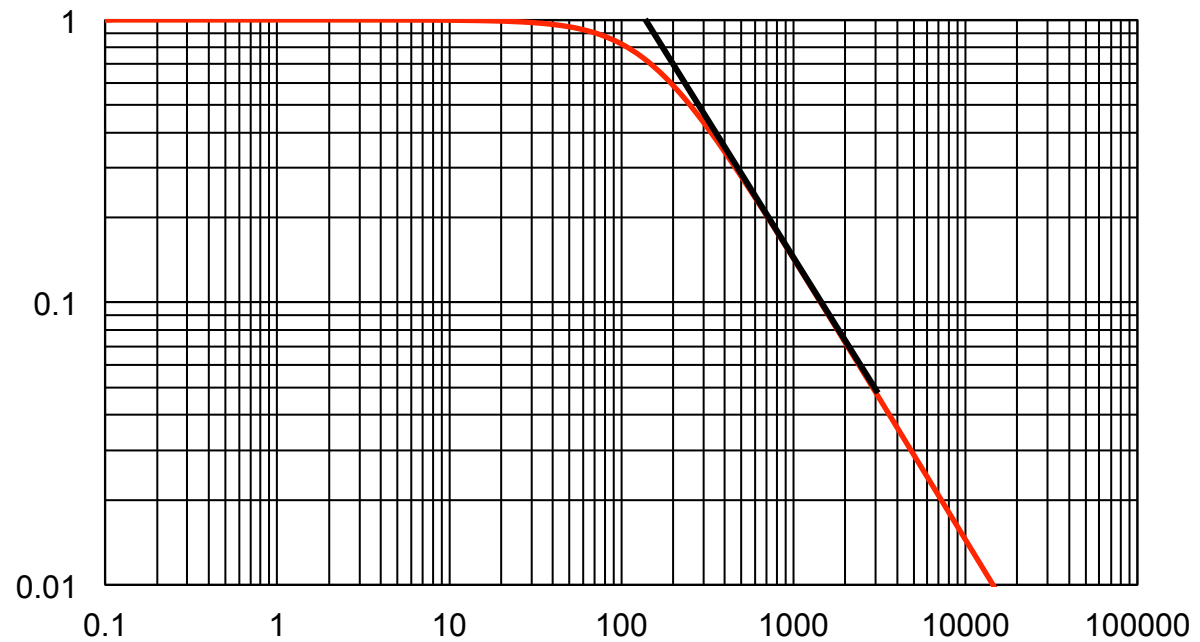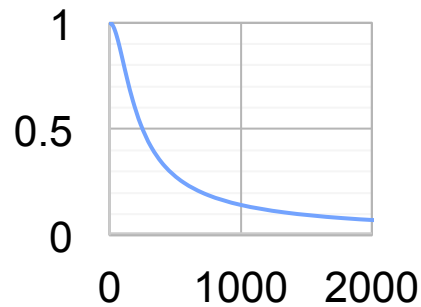$2\pi RC$  is about 7ms;  $F_c = 140\text{Hz}$





# High-Pass



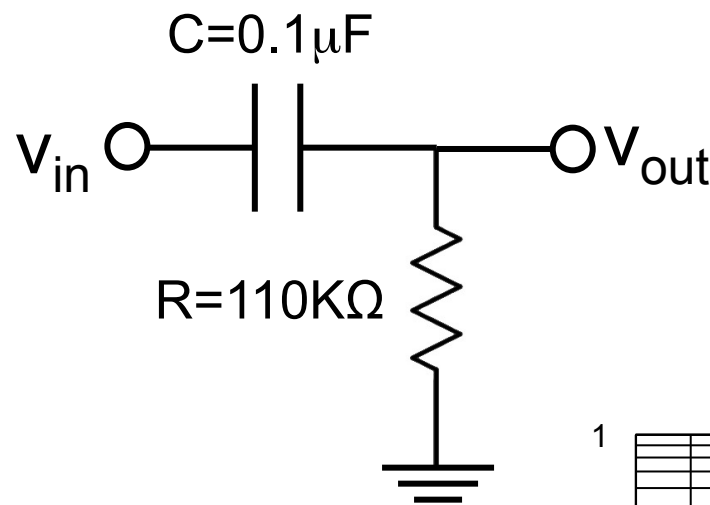


$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j*2\pi FC}} = \frac{j*2\pi FRC}{1 + j*2\pi FRC}$$

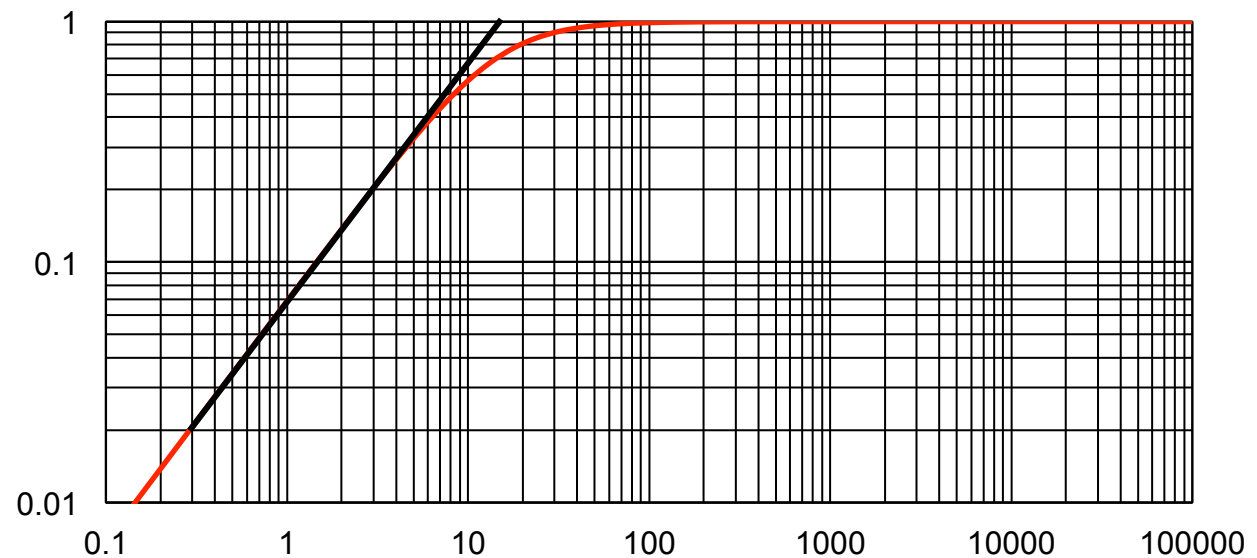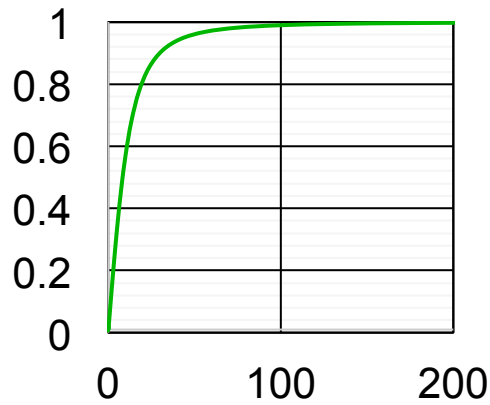$2\pi RC$  is about 70ms;  $F = 14\text{Hz}$


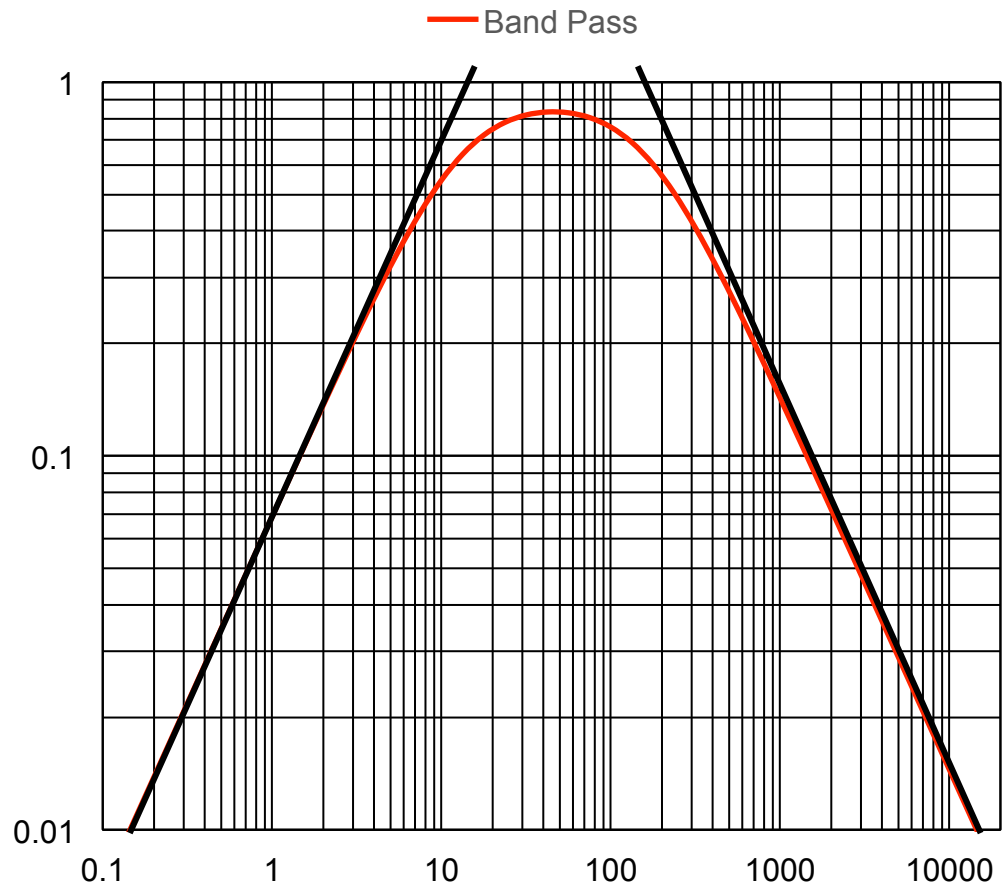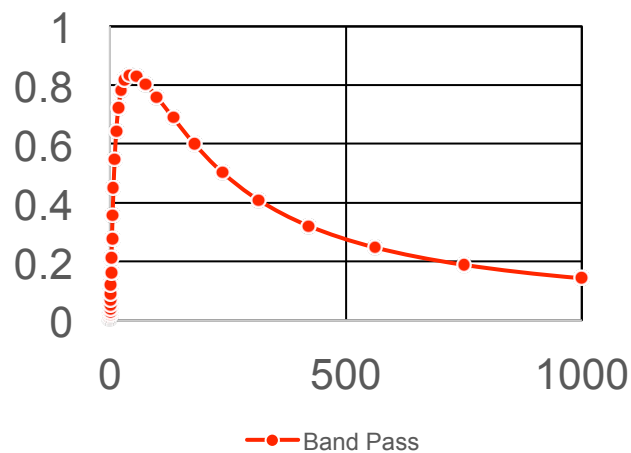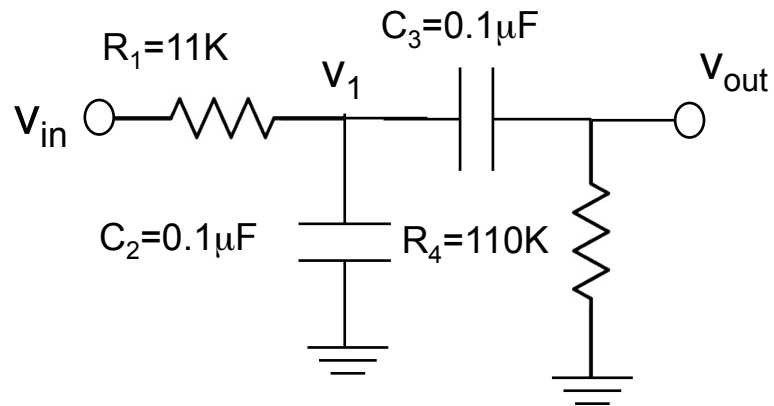
# Band Pass – Combining the Low and High Pass



# One More Trick With Log-Log Plots


- Remember:

$$\log(A*B) = \log(A) + \log(B), \text{ and } \log(A/B) = \log(A) - \log(B)$$

- So: 
$$\frac{V_{out}}{V_{in}} = \frac{j*2\pi FRC}{1 + j*2\pi FRC}$$

- Can add two lines

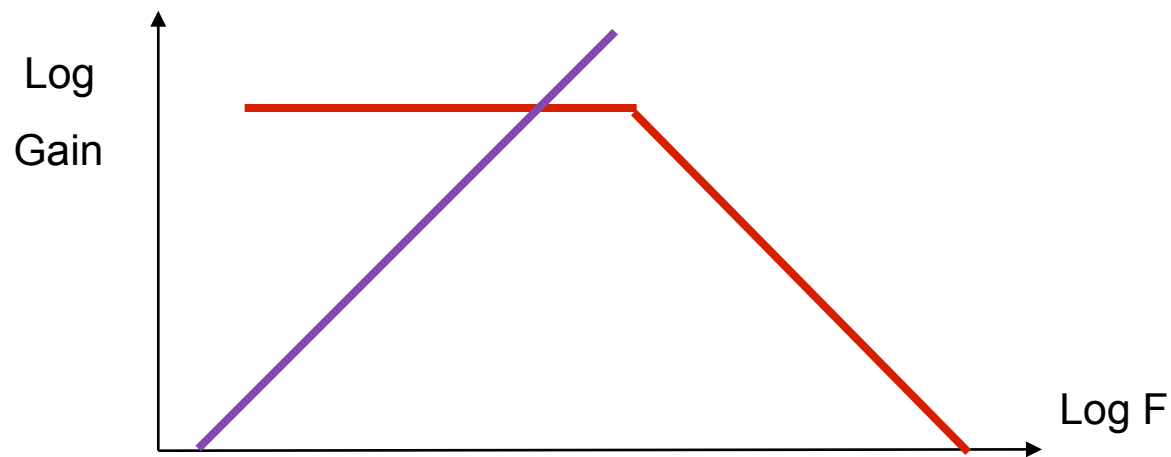- One slope +1
- One flat and then slope -1




## Log-Log Plot Tricks, cont'd

- Our bandpass filter earlier had a gain function of the form

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{j * 2\pi F R_2 C_2}{1 + j * 2\pi F (R_1 C_1 + R_2 C_2) + (j * 2\pi F)^2 R_1 C_1 R_2 C_2}$$

- If we can factor the polynomial, then we can add lines as on the last slide
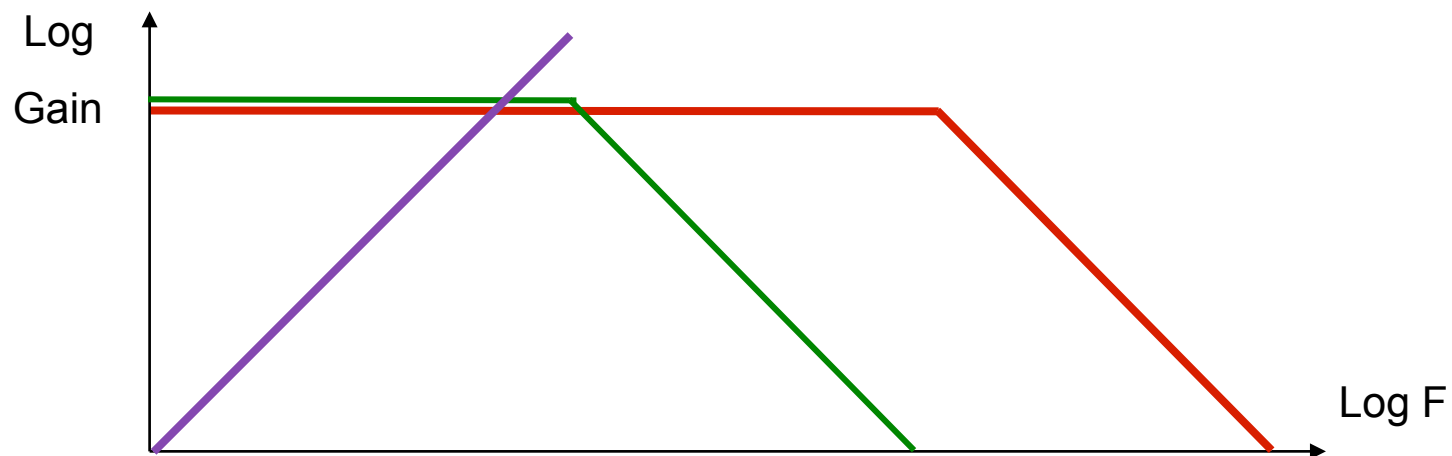
$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{j * 2\pi F R_2 C_2}{(1 + j * 2\pi F R_1 C_1) * (1 + j * 2\pi F R_2 C_2)}$$






---

**dB**
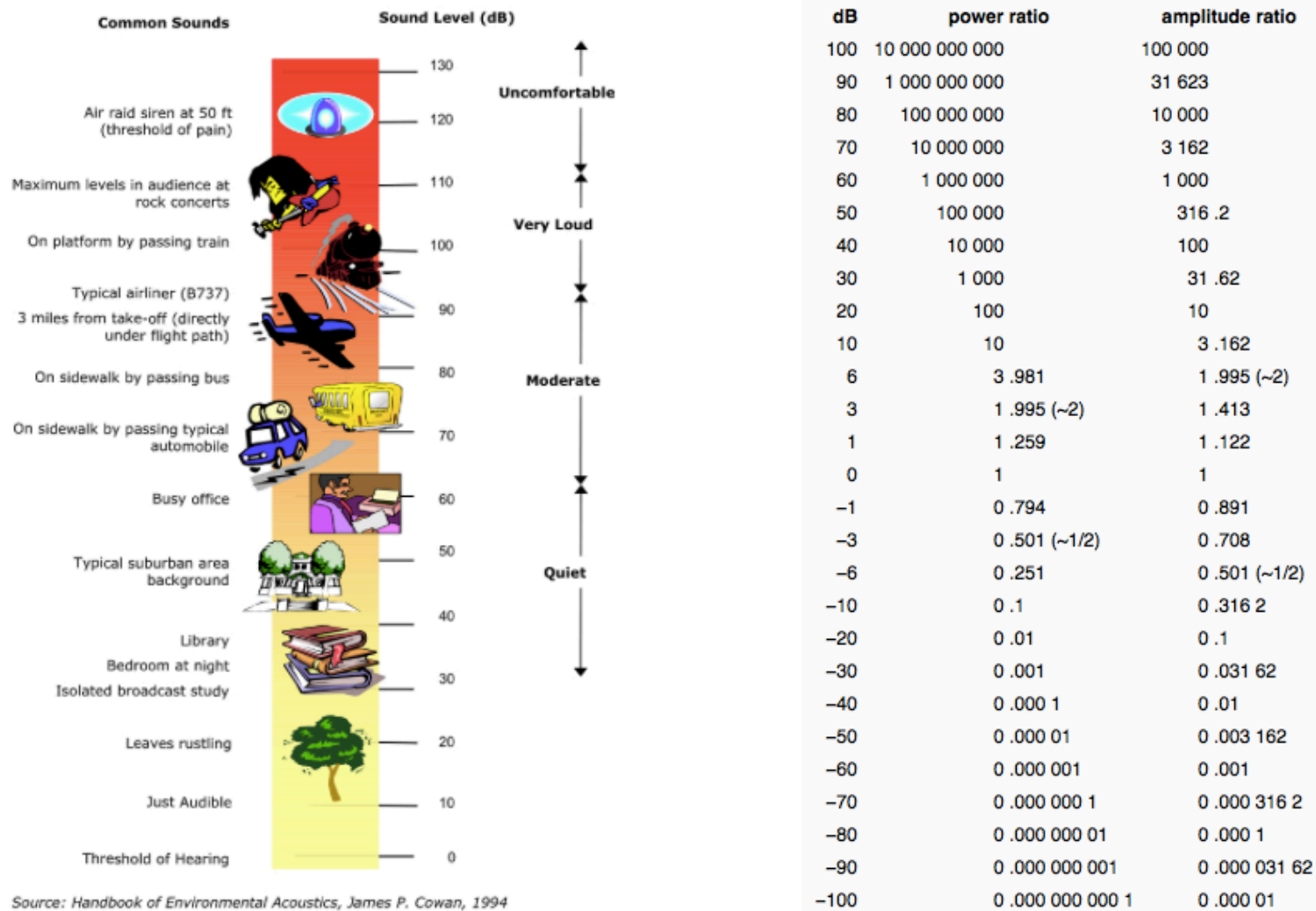
# Use of Logarithmic Scales to Represent Wide Ranges



# dB

---

- In many places you will see the symbol **dB**
  - This is decibel
  - It is a logarithmic measure of power gain
    - $\text{dB} = 10 * \log (\text{Power}_{\text{out}}/\text{Power}_{\text{in}})$
- It is logarithmic so
  - 10dB is a 10x change in power
  - 20dB is a 100x change in power
  - 3dB is a 2x change in power
- Since power is proportional to  $V^2$ 
  - A 10x change in voltage is a 100x change in power
    - This is a 20dB change
  - 6dB is a 2x change in voltage


# Plotting Gain vs. Frequency

---

- Want to plot  $\log(\text{gain})$  vs.  $\log(\text{frequency})$
- dB is already log of the gain
  - So the plots look semilog
    - Log of frequency in the x direction
    - dB in the y direction
  - But this is the log-log plot that we want
- Please remember that dB measures power
  - 10x in voltage = 20dB
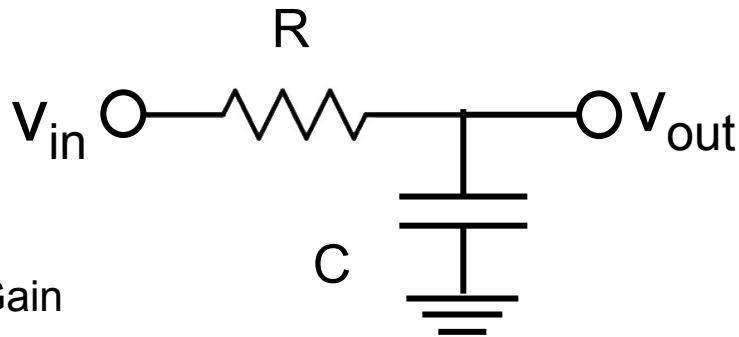
# Plotting dB vs. Frequency


- Consider the simple low pass filter we looked at earlier




$$\text{Gain} = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{1 + j * 2\pi FRC} = \frac{1}{1 + jF / F_c}$$

$$\begin{aligned}\text{Gain}_{\text{dB}} &= 20\log_{10}\left(\frac{1}{1 + jF / F_c}\right) \\ &= 20\log_{10}(1) - 20\log_{10}(1 + jF / F_c) \\ &\cong 0 - 20\log_{10}(F / F_c)\end{aligned}$$

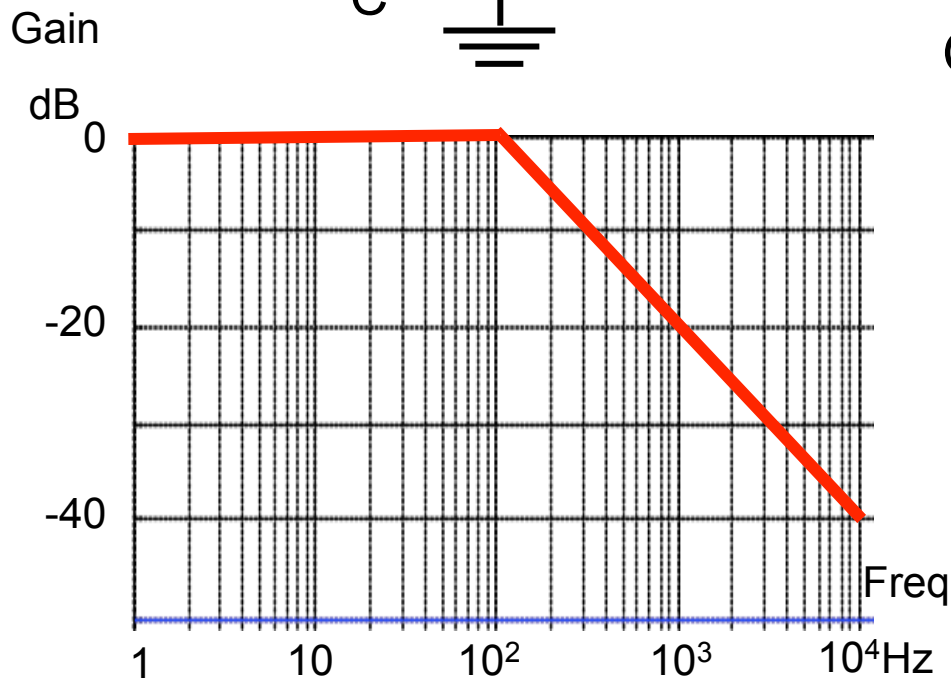(assuming F is large and neglecting the phase)



# FYI – Hendrik Bode


<b>Hendrik Wade Bode</b>	
	
Hendrik Wade Bode	
<b>Born</b>	December 24, 1905 <a href="#">Madison, Wisconsin</a>
<b>Died</b>	June 21, 1982 (aged 76) <a href="#">Cambridge, Massachusetts</a>
<b>Residence</b>	<a href="#">Cambridge, Massachusetts</a>
<b>Nationality</b>	American
<b>Fields</b>	<a href="#">Control Systems</a> , <a href="#">Physics</a> , <a href="#">Mathematics</a> , <a href="#">Telecommunications</a>
<b>Institutions</b>	<a href="#">Ohio State University</a> <a href="#">Bell Laboratories</a> <a href="#">Harvard University</a>
<b>Alma mater</b>	<a href="#">Ohio State University</a> <a href="#">Columbia University</a>
<b>Known for</b>	<a href="#">Bode plot</a> , <a href="#">Control theory</a> , <a href="#">Telecommunications</a>
<b>Notable awards</b>	<a href="#">Richard E. Bellman Control Heritage Award</a> (1979) <a href="#">Rufus Oldenburger Medal</a> (1975) <a href="#">President's Certificate of Merit</a> <a href="#">Edison Medal</a> (1969) <a href="#">Ernest Orlando Lawrence Award</a> (1960)

- Bode (1905 –1982) spent most of his career at Bell Labs.
- He worked on control system theory and electronic filters and during WW II he worked on using radar information to direct anti-aircraft guns to try to intercept enemy aircraft and missiles like the German V2 missile.
- But today he's best remembered for inventing Bode plots used to describe the frequency behavior of linear systems.

(Wikipedia)

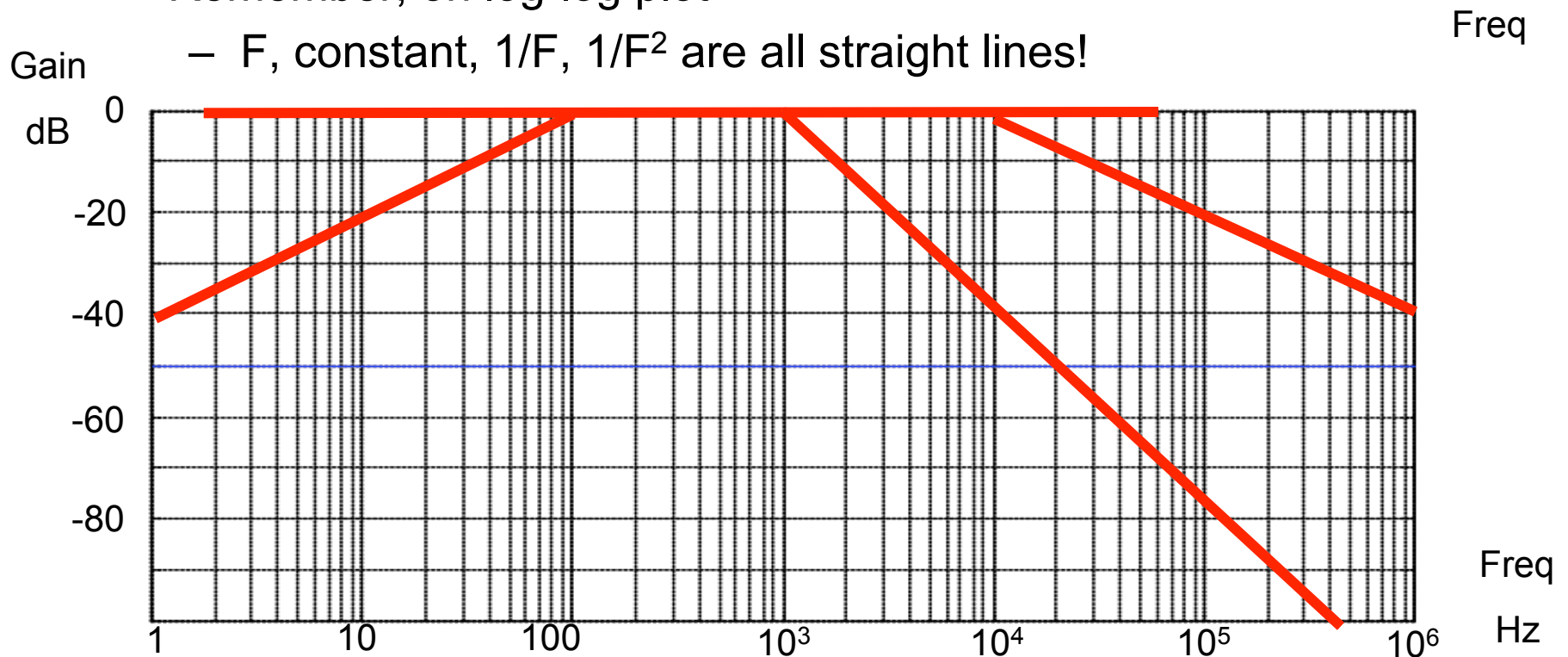
# Plotting the Output

- We use a Bode Plot to plot the transfer function of a circuit
  - Remember that this is the log of gain vs. log of frequency
- Remember, on log-log plot
  - $F$ , constant,  $1/F$ ,  $1/F^2$  are all straight lines!


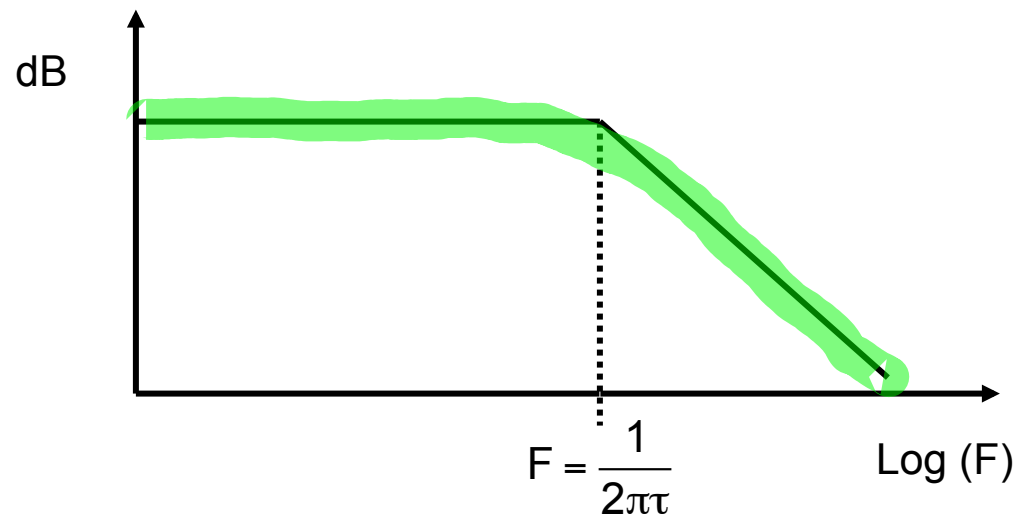
# Circuit Bode Plots


- These are generally easy to draw
  - Know the slopes at different frequency ranges
    - Plot those straight lines
  - These lines will intercept at the  $F$  where the terms are equal  
i.e.  $F = 1/2\pi\tau = 1/2\pi RC$



- Actual curve will be close to the straight lines



## Example

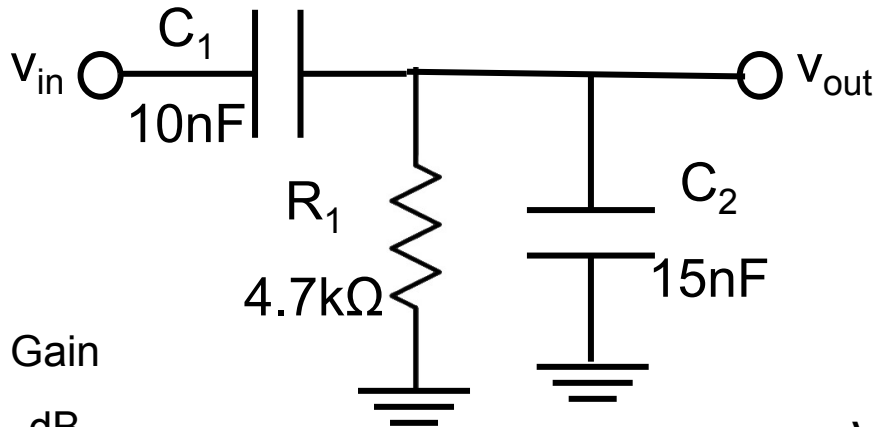


$$\frac{V_{out}}{V_{in}} = \frac{Z_{R1} \parallel Z_{C2}}{Z_{C1} + Z_{R1} \parallel Z_{C2}}$$

$$Z_{R1} \parallel Z_{C2} = \frac{Z_{R1} * Z_{C2}}{Z_{R1} + Z_{C2}} = \frac{R_1}{1 + 2\pi f R_1 C_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{R_1}{1 + 2\pi f R_1 C_2}}{\frac{1}{2\pi f C_1} + \frac{R_1}{1 + 2\pi f R_1 C_2}} = \frac{2\pi f R_1 C_1}{1 + 2\pi f R_1 (C_1 + C_2)}$$

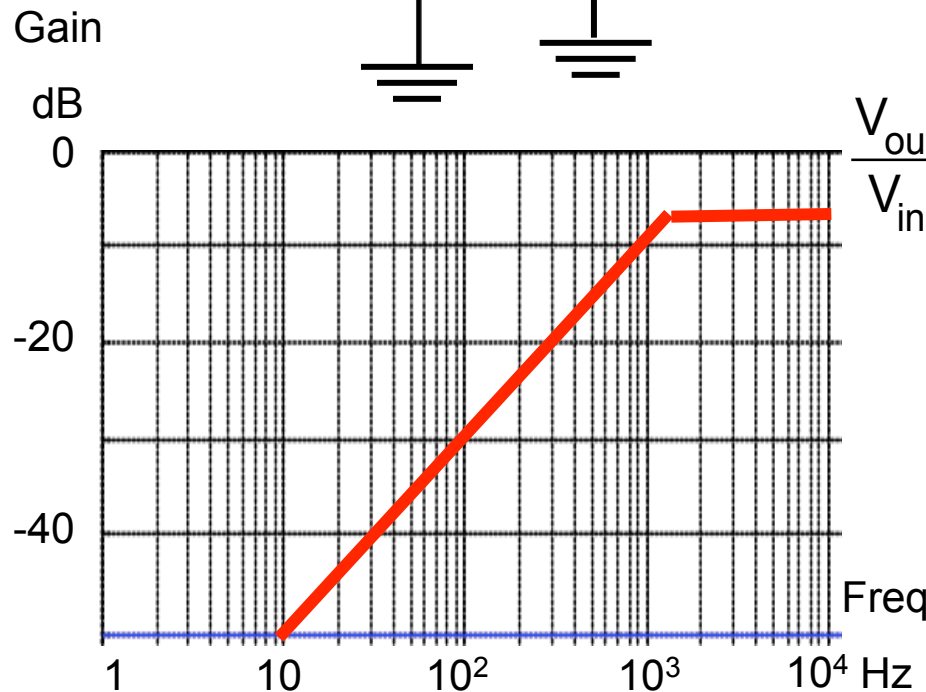
$$F_c = \frac{1}{2\pi R_1 (C_1 + C_2)} = 1.35 \text{ kHz}$$



$$\text{Gain}_{dB} @ \text{HighF} = 20 \log \left( \frac{C_1}{C_1 + C_2} \right) = -7.96 \text{ dB}$$

# EveryCircuit – Frequency Resonse

---

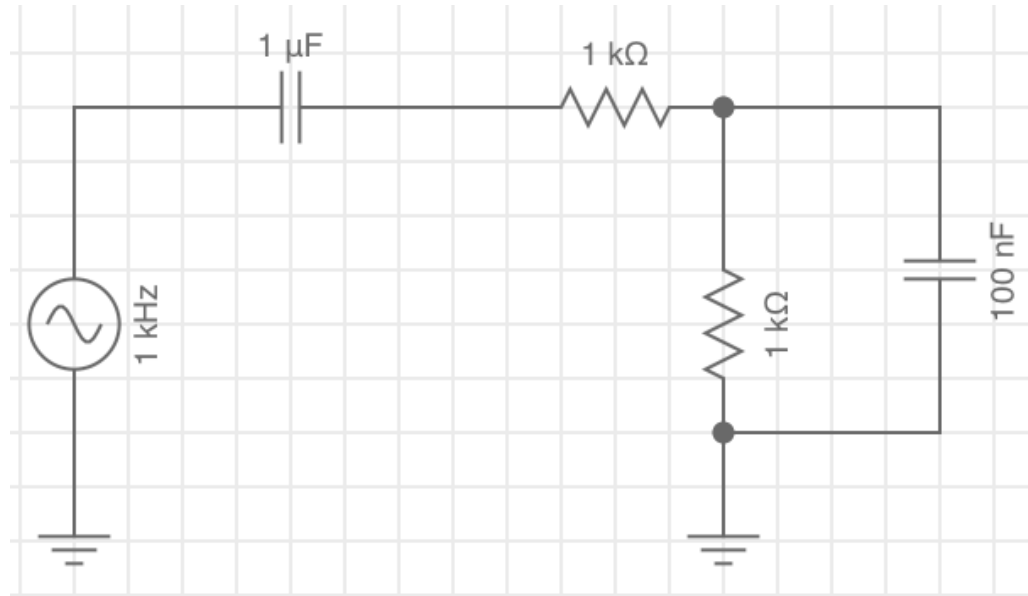

- EveryCircuit can be used to calculate and plot Bode plots for circuits. We'll demo this in class.
- This is very useful for checking answers to HW problems or for developing understanding about circuit frequency response.


Bonus Section (Not on HW, Exams)  
See Class Reader For Details

---

**WHAT DOES  $(1 + j*x)$  REALLY  
MEAN?**


# An Example - High Pass RC Filter
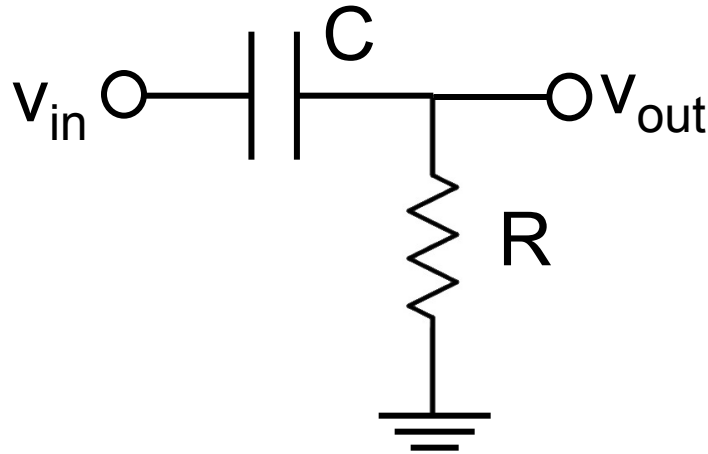
## Bonus Material – See Class Reader For Details



$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j * 2\pi FC}} = \frac{j * 2\pi FRC}{1 + j * 2\pi FRC}$$
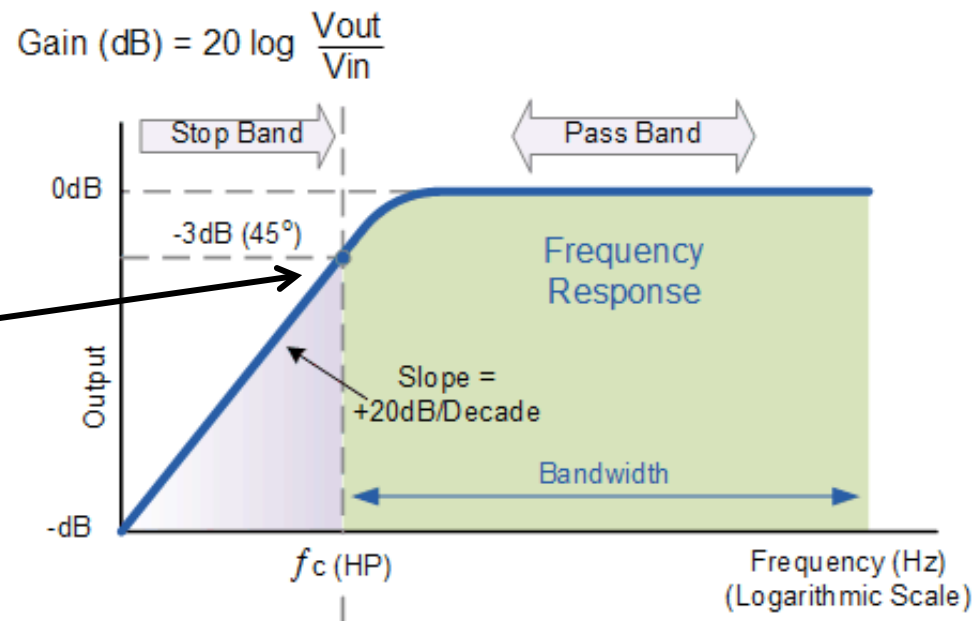
$$2\pi FRC = 1 \text{ or } F = \frac{1}{2\pi RC}$$



(Electronic Tutorials)

## 3dB?

### Bonus Material – See Class Reader For Details

---

- Notice that when the two terms are the same,  $F = 1/2\pi RC$ 
  - The overall gain is -3dB
  - This might seem right since -3dB is  $1/2$ , BUT
  - This is the power ratio!
    - The voltage ratio is only  $1/\sqrt{2}$  !
- What is going on?
- To understand, we'll need to think about what  $(1 + j\omega x)$  means

# Adding Sine and Cosine Waveforms

## Bonus Material – See Class Reader For Details

---

- $1 + j*x$  means the waveform is the sum of
  - A sinewave with amplitude 1
  - With a cosine wave with amplitude “x”
- The good news is that this always results in a sinusoidal waveform
  - With some phase shift between a sin and cos (+90°)
  - So we can write

$$A \sin(2\pi Ft + \phi) = \sin(2\pi Ft) + x * \cos(2\pi Ft)$$

- And we want to find A and  $\phi$

# The Trick

## Bonus Material – See Class Reader For Details

---

$$C * \sin(2\pi Ft + \phi) = A * \sin(2\pi Ft) + B * \cos(2\pi Ft)$$

- This equation is always true so
  - At  $t = 0$ , the sine term is zero


$$C * \sin(\phi) = B$$

- At  $t = 1/(4F)$ , the cosine term is zero, so

$$C * \cos(\phi) = A$$

- So the amplitude of the resulting sine wave is

$$\sqrt{A^2 + B^2}$$

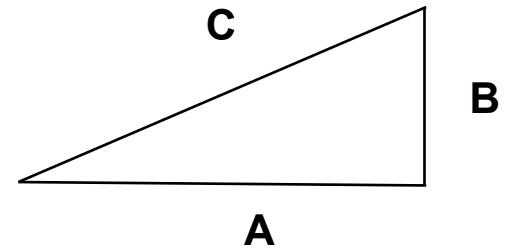

# Learning Objectives For Today

---

- Understand how to create Bode plots for RC circuits
  - You plot two straight lines that intercept at  $F=1/2\pi RC$
- (Bonus Section) Understand what an amplitude of  $(1+ j*2\pi RCF)$  means
  - The result is a sum of a sine and cosine wave