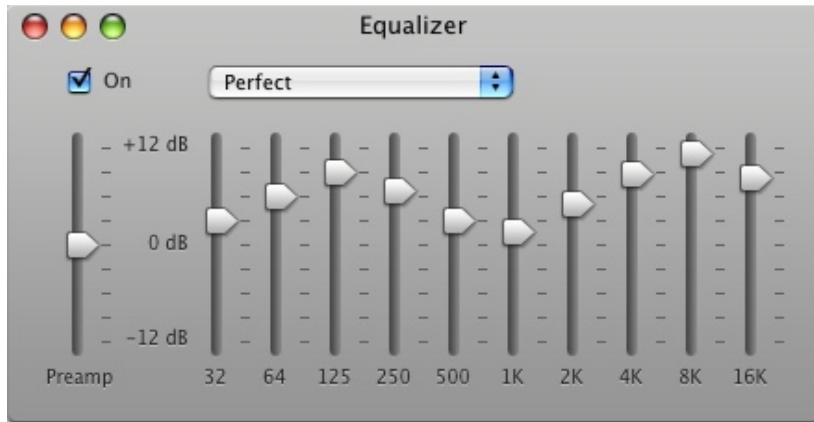

E40M Capacitors


Reading

- Reader:
 - Chapter 6 – Capacitance
- A & L:
 - 9.1.1, 9.2.1


Why Are Capacitors Useful/Important?



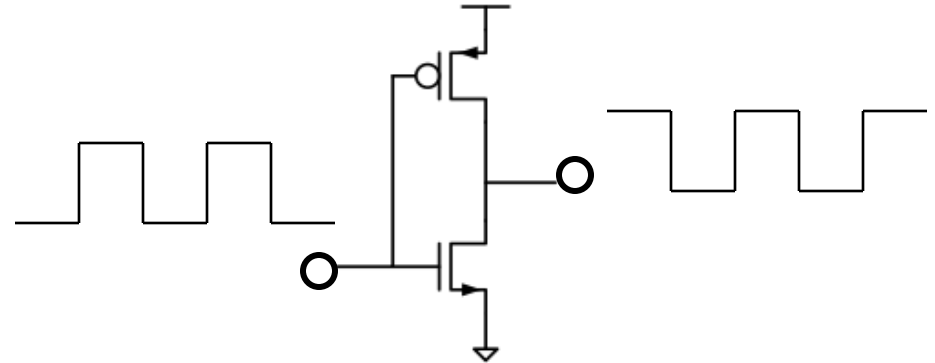How do we design circuits that respond to certain frequencies?



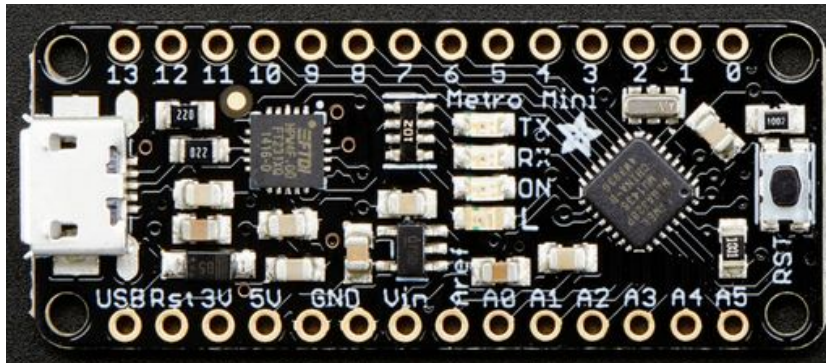
What determines how fast CMOS circuits can work?




Why do we often put a large "bypass" capacitor between Vdd and Gnd?

Capacitors

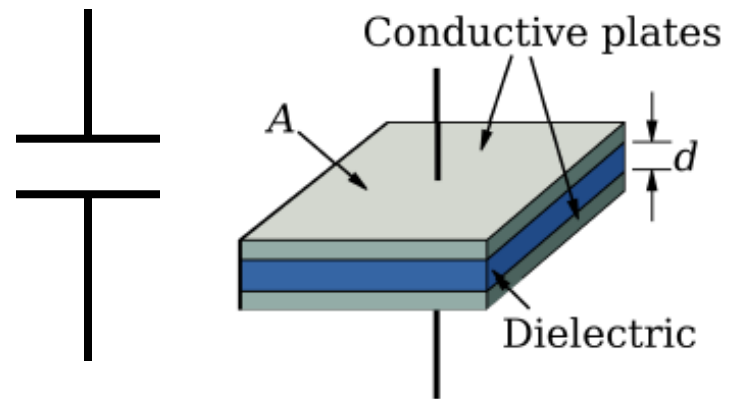- What is a capacitor?
 - It is a new type of two terminal device
 - It is linear
 - Double V , you will double I
 - We will see it doesn't dissipate energy
 - Stores energy




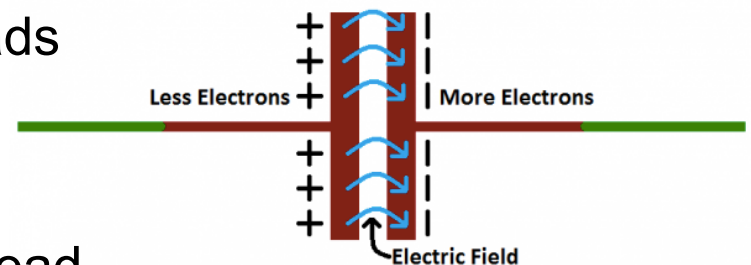- Rather than relating i and V
 - Relates Q , the charge stored on each plate, to Voltage
 - $Q = CV$
 - Q in Coulombs, V in Volts, and C in Farads
- Like all devices, it is always charge neutral
 - Stores $+Q$ on one lead, $-Q$ on the other lead



iV for a Capacitor

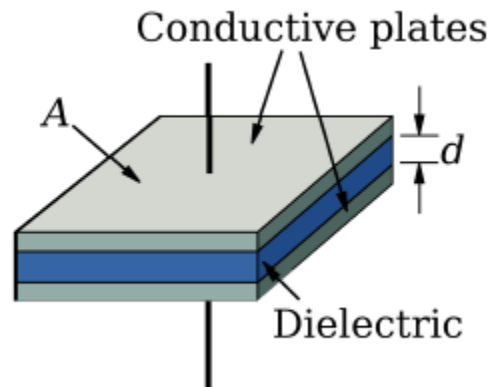- We generally don't work in Q , we like i and V
 - But current is charge flow, or dQ/dt
- So if $Q = CV$, and $i = dQ/dt$
 - $i = C dV/dt$
- This is a linear equation but between i and dV/dt . If you double i for all time, dV/dt will also double and hence V will double.




$$C = \frac{\epsilon A}{d}$$

where ϵ is the dielectric constant

Capacitors Only Affect Time Response not Final Values

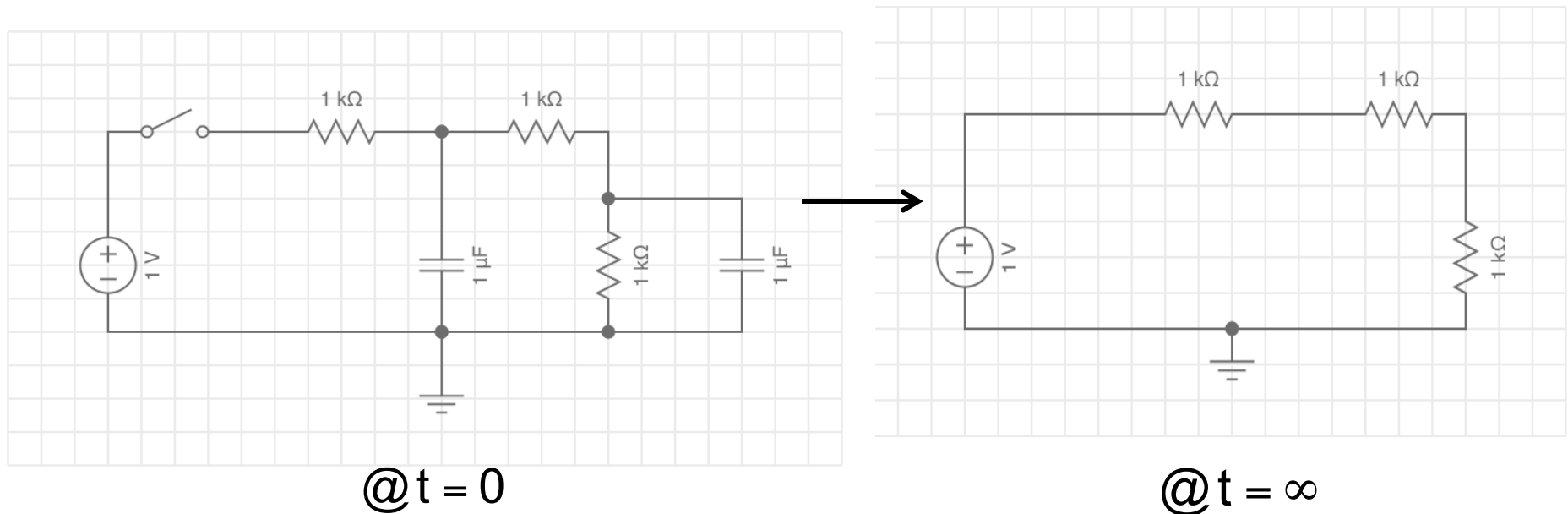- Capacitors relate i to dV/dt
- This means if the circuit “settles down” and isn’t changing with time, a capacitor has no effect (looks like an open circuit).



So What Do Capacitors Do?

- They affect how fast a voltage can change
 - Current sets dV/dt , and not V
 - Fast changes require lots of current
- For very small Δt capacitors look like voltage sources
 - They can supply very large currents
 - And not change their voltage
- But for large Δt
 - Capacitors look like open circuits (they don't do anything)

Capacitor Energy

- The Power that flows into a charging capacitor is


$$P = iV = \left(C \frac{dV}{dt} \right) V$$

- And the energy stored in the capacitor is

$$E = \int P dt$$

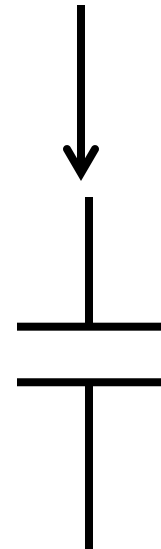
$$\therefore E = \int P dt = \int_0^V C V dV = \frac{1}{2} C V^2$$




- This energy is stored and can be released at a later time. No energy is lost.



Capacitor Types

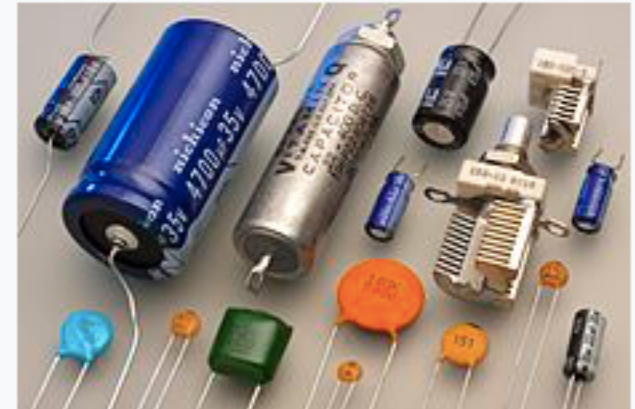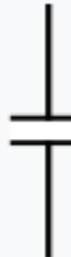- There are many different types of capacitors
 - Electrolytic, tantalum, ceramic, mica, . . .
- They come in different sizes
 - Larger capacitance
 - Generally larger size
 - Higher voltage compliance
 - Larger size
- Electrolytic have largest cap/volume
 - But they have limited voltage
 - They are polarized
 - One terminal must be + vs. other




Type	Passive		
Invented	Ewald Georg von Kleist		
	Electronic symbol		
			
	Fixed Capacitor	Polarized Capacitor	Variable Capacitor

http://en.wikipedia.org/wiki/Types_of_capacitor



Gate of MOS Transistor

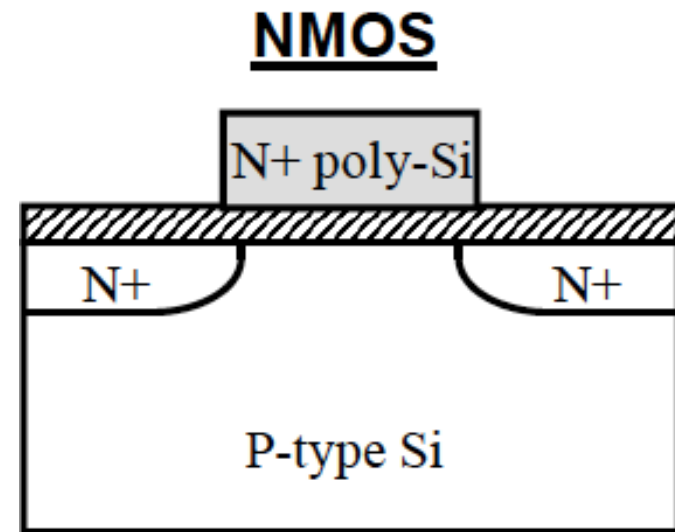- Is a capacitor between Gate and Source
- To change the gate voltage
 - You need a current pulse (to cause dV/dt)
- If the current is zero (floating)
 - $dV/dt = 0$, and the voltage remains what it was!




All Real Wires Have Capacitance

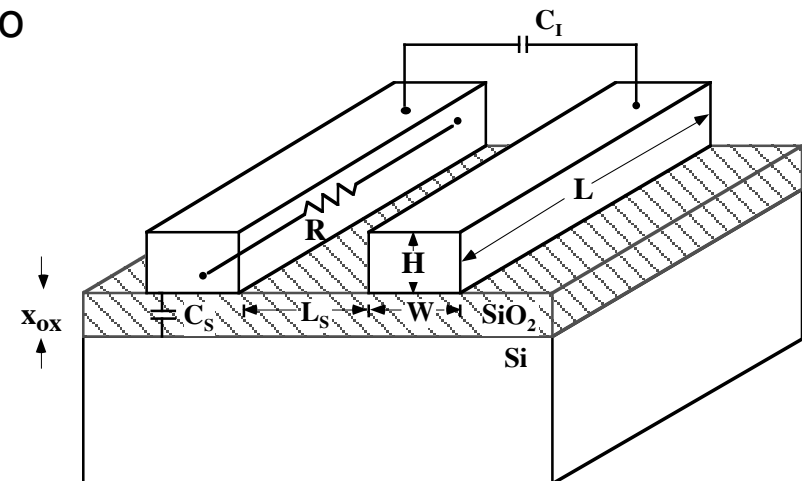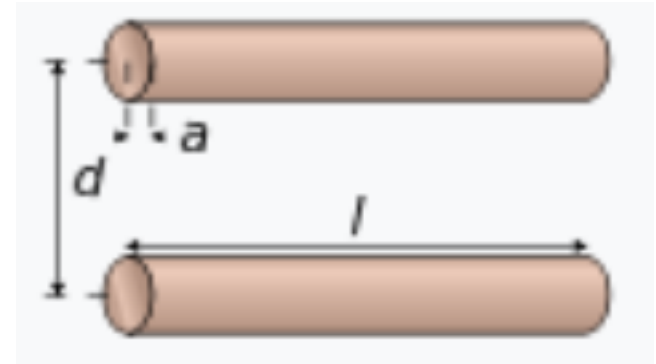- It will take some charge to change the voltage of a wire
 - Think back to our definition of voltage
 - Potential energy for charge
 - To make a wire higher potential energy
 - Some charge has to flow into the wire, to make the energy higher for the next charge that flows into it
- This capacitance is what sets the speed of your computer
 - And determines how much power it takes!





Capacitor Info, If You Know Physics E&M...



- Models the fact that energy is stored in electric fields
 - Between any two wires that are close to each other
- A capacitor is formed by two terminals that are not connected
 - But are close to each other
 - The closer they are, the larger the capacitor
- To create a voltage between the terminals
 - Plus charge is collected on the positive terminal
 - Negative charge is collected on the negative terminal
- This creates an electric field (Gauss's law)
 - Which is what creates the voltage across the terminals
 - There is energy stored in this electric field

 

Capacitors in Parallel and Series

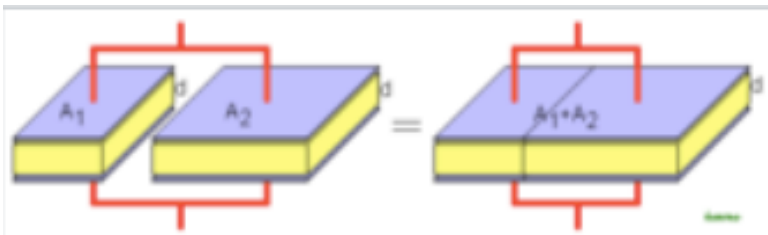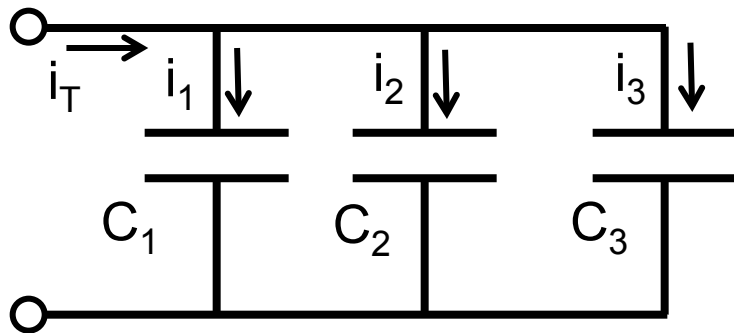


Capacitors in Parallel and Series

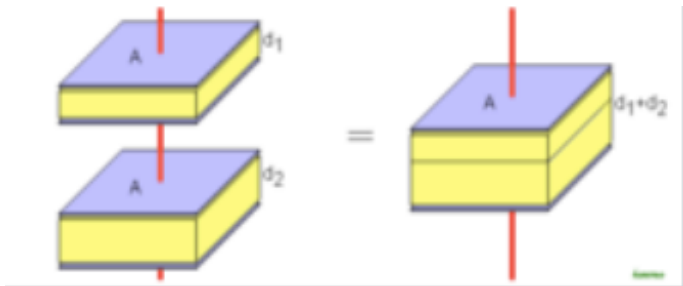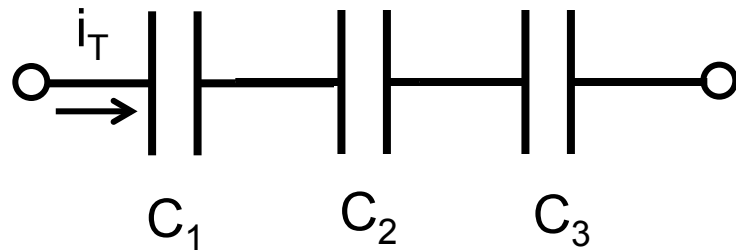

CAPACITOR RESISTOR CIRCUITS

Capacitors and Logic Gate Speeds

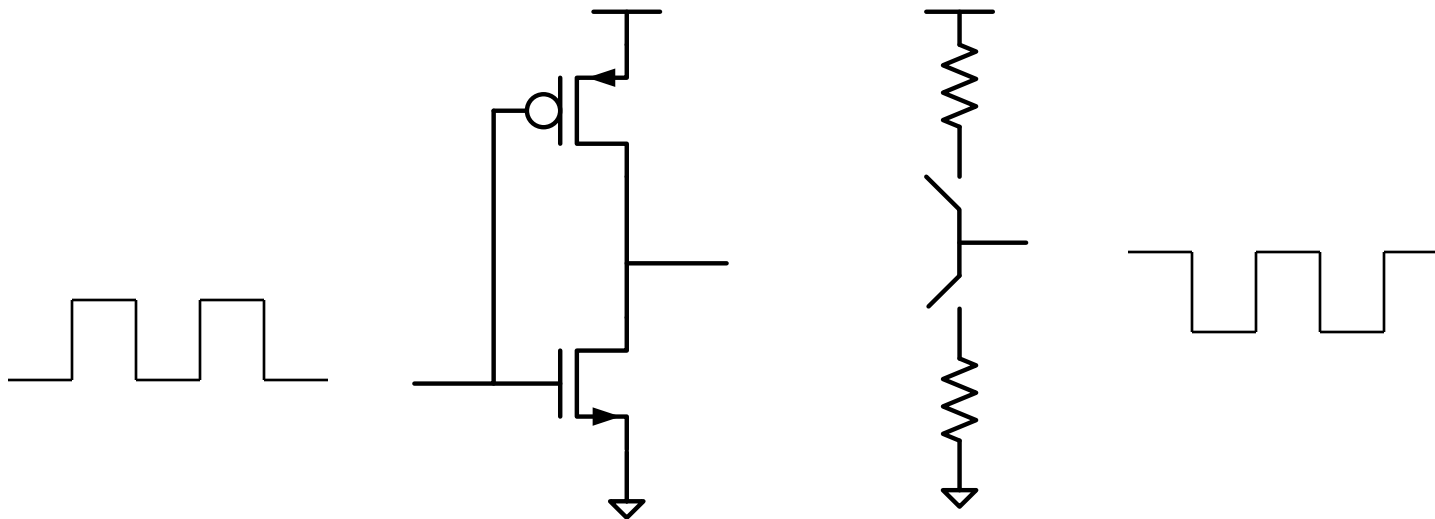- When the input changes from low to high
 - The pMOS turns off, and the nMOS turns on
 - The output goes from high to low
- But in this model
 - The output changes as soon as the input changes





Gates Are NOT Zero Delay

- It would be great if logic gates had zero delay
 - But they don't
- Fortunately, it is easy to figure out the delay of a gate
 - It is just caused by the transistor resistance
 - Which we know about already
 - And the transistor and wire capacitance

Improved Model

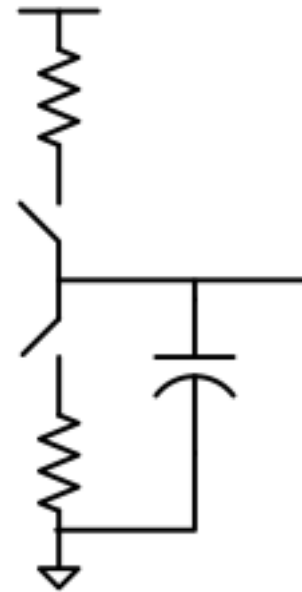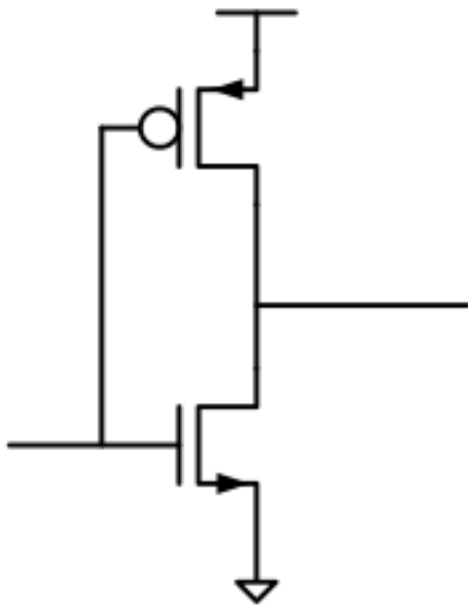- Just add a capacitor to the output node
 - Its value is equal to the capacitance of the gates driven
 - Plus the capacitance of the wire itself




RC Circuit Equation

- When the input to the inverter is low, the output will be at V_{dd}
 - Right after the input rises, here is the circuit

- Want to find the capacitor voltage verses time

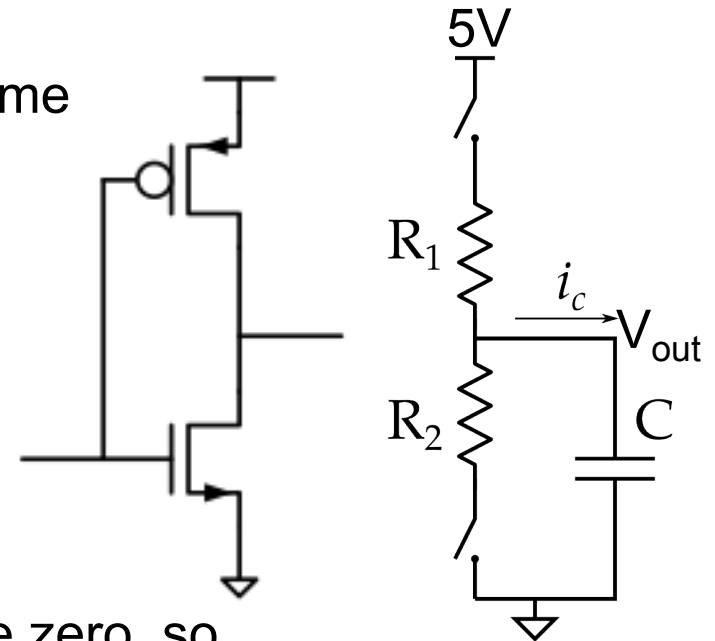- Just write the nodal equations:
 - We just have one node voltage, V_{out}
 - $i_{RES} = V_{out}/R_2$
 - $i_{CAP} = C dV_{out}/dt$




- From KCL, the sum of the currents must be zero, so

$$\frac{dV_{out}}{dt} = -\frac{V_{out}}{R_2 C}$$

RC Circuit Equations

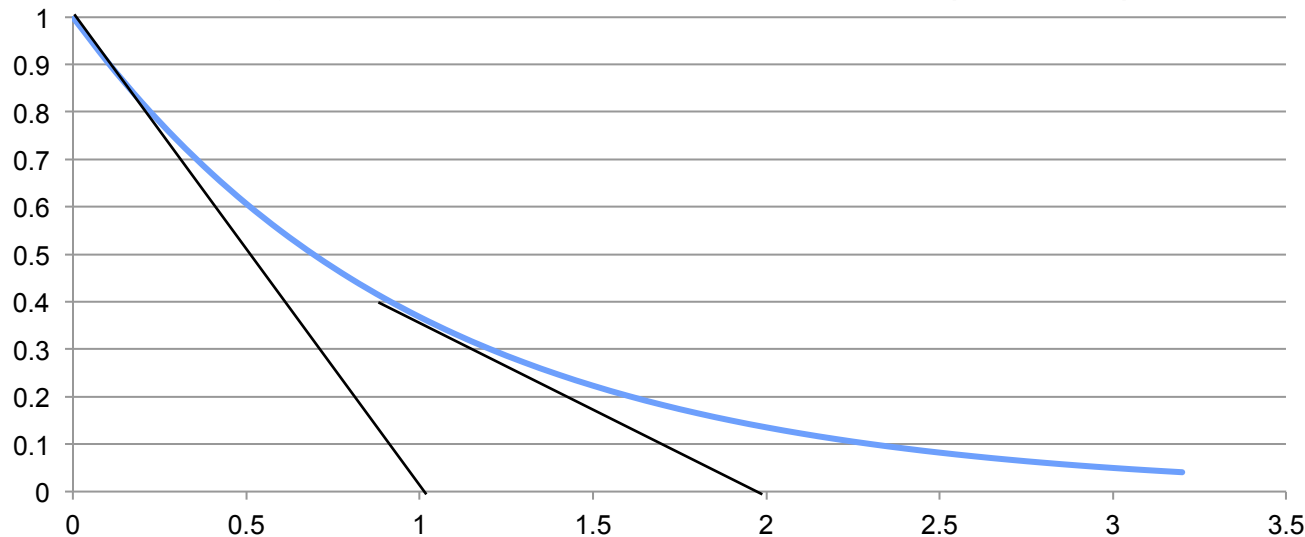- Solving, $\int_5^V \frac{dV_{\text{out}}}{V_{\text{out}}} = -\int_0^t \frac{dt}{R_2 C}$ so that $\ln(V_{\text{out}}) - \ln(5V) = -\frac{t}{R_2 C}$
- This is an exponential decay
 - The x axis is in time constants $\therefore V_{\text{out}} = 5V \left(e^{-t/R_2 C} \right)$
 - The y axis has been normalized to 1
 - Slope always intersects 0 one tau later ($\tau = RC$)




What Happens When Input Falls?

- Now the voltage across the capacitor starts at 0V
 - $i = (V_{dd} - V_{out})/R_1$
 - $dV_{out}/dt = i/C$


$$\frac{dV_{out}}{dt} = \frac{(V_{dd} - V_{out})}{R_1 C}$$

- Not quite the right form
 - Need to fix it by changing variables
 - Define $V_{new} = V_{dd} - V_{out}$
 - $dV_{out}/dt = -dV_{new}/dt$, since V_{dd} is fixed
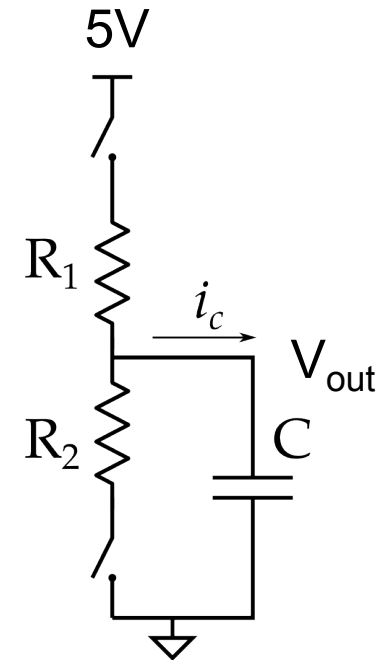
$$\int_5^V \frac{dV_{new}}{V_{new}} = -\int_0^t \frac{dt}{R_1 C} \quad \text{so that} \quad \ln(V_{new}) - \ln(5) = -\frac{t}{R_1 C} \quad \therefore V_{out} = 5V \left(1 - e^{-t/R_1 C}\right)$$




RC Circuits in the Time Domain

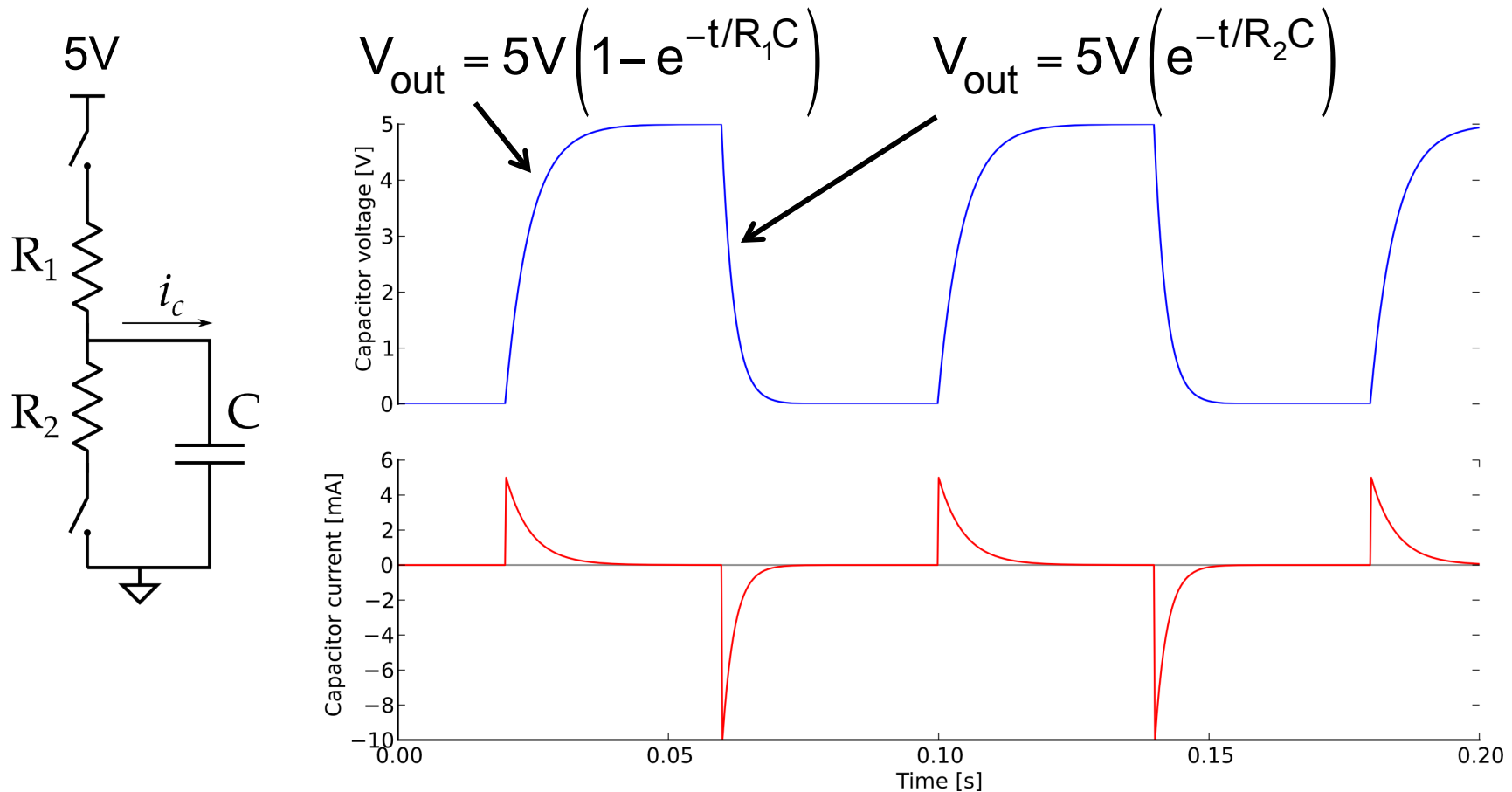


In capacitor circuits, voltages change “slowly”, while currents can be instantaneous.

Simple RC Circuit Demo

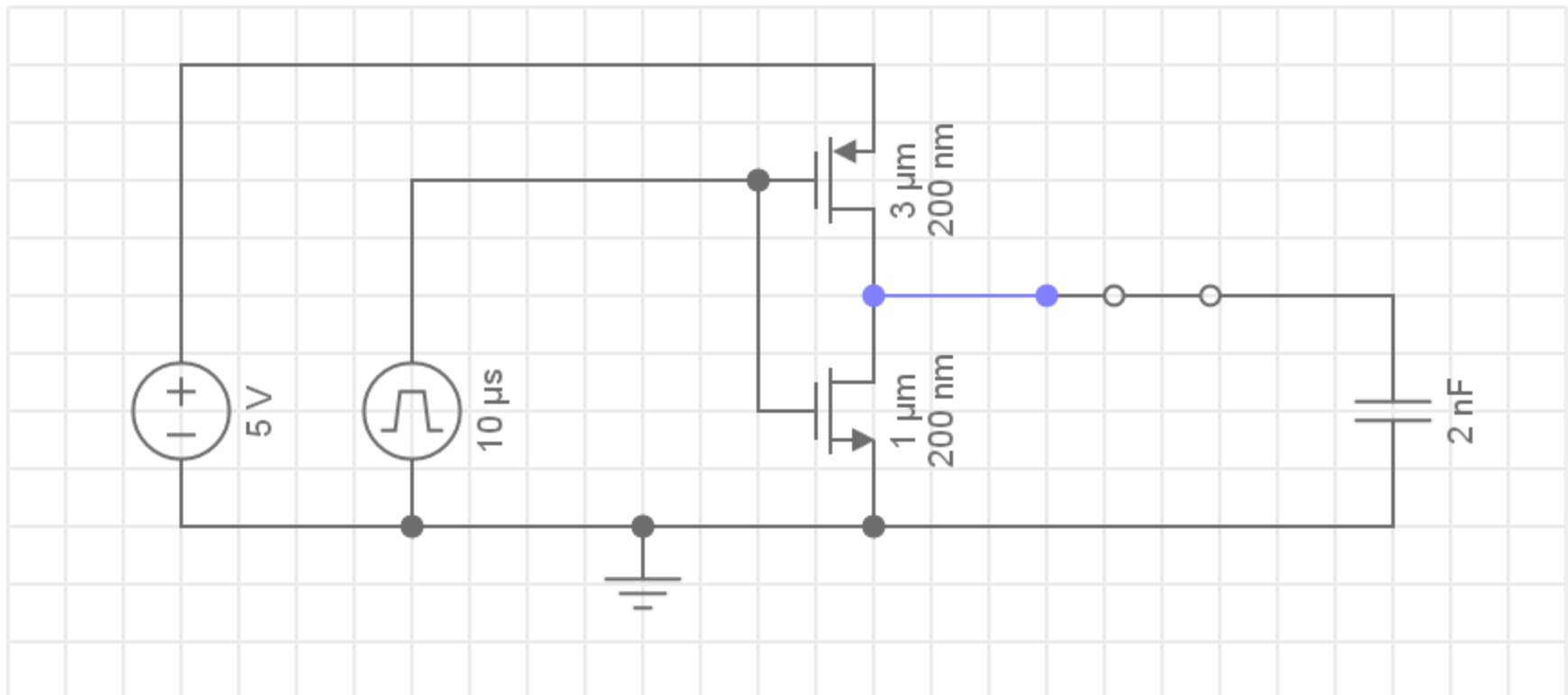


EveryCircuit Demo – CMOS Inverter

Interesting Aside

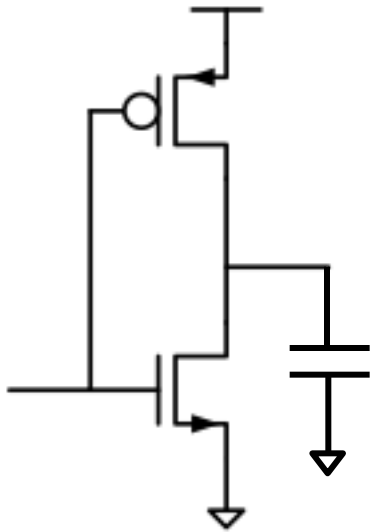

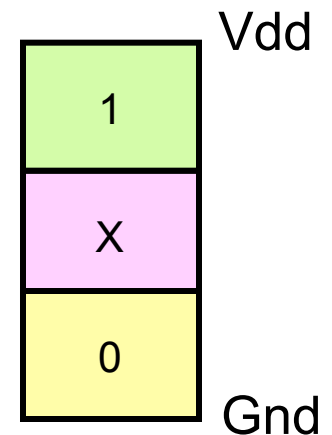- Exponentials “never” reach their final value
- So if this logic gate is driving another gate, when does the next gate think its input is 0 or 1?
- This is one of the reasons why logic levels are defined as a range of values.



Learning Objectives

- Understand what a capacitor is
 - $i = C \, dV/dt$
 - It is a device that tries to keep voltage constant
 - Will supply current (in either direction) to resist voltage changes
- Understand how voltages and current change in R C circuits
 - Voltage waveforms are continuous
 - Takes time for their value to change
 - Exponentially decay to final value (the DC value of circuit)
 - Currents can change abruptly
- In the next few lectures we'll return to representing signals in the frequency domain and learn about a new way to solve capacitor circuits.